

# From Nand to Tetris
 
## **Building a Modern Computer From First Principles**



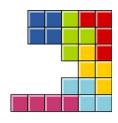

Home	
Projects	
Book	
Software	
Demos	
License	
Cool Stuff	
Team	
Stay in Touch	
Q&A	

# **Project 5: Computer Architecture**

### Background

In previous projects we've built the computer's basic processing and storage devices (ALU and RAM, respectively). In this project we will put everything together, yielding the complete Hack Hardware Platform. The result will be a general-purpose computer that can run programs written in the Hack machine language.

#### Objective

Complete the construction of the Hack CPU and the Hack hardware platform, leading up to the top-most Computer chip.

## Chips

Chip Name	Description	Testing
Chip Name	Description	Testing
Memory.hdl	Entire RAM address space	Test your chip using the supplied Memory.tst and Memory.cmp files.
Chip Name CPU.hdl	Description The Hack CPU	Test your chip using the supplied CPU.tst and CPU.cmp files.
		Alternative test files (less thorough but do not require using the built-in DRegister) are supplied in CPU-external.tst and CPU-external.cmp.
Chip Name	Description	Testing
Computer.hdl	hdl The platform's top-most chip	Test by running some Hack programs on the constructed chip. See more instructions below.

#### Contract

The computer platform that you build should be capable of executing programs written in the Hack machine language, specified in Chapter 4. Demonstrate this capability by having your Computer chip run the three test programs given below.

#### Testing

**Testing the Memory and CPU chips:** It's important to unit-test these chips before proceeding to build the overall Computer chip. Use the test scripts and compare files listed above.

Testing the Computer chip: A natural way to test the overall Computer chip implementation is to have it execute some sample programs written in the Hack machine language. In order to perform such a test, one can write a test script that (i) loads the Computer.hdl chip description into the supplied Hardware Simulator, (ii) loads a machine-level program from an external .hack file into the ROM chip-part of the loaded Computer.hdl chip, and then (iii) runs the clock enough cycles to execute the loaded instructions. We supply all the files necessary to run three such tests, as follows:

Program Comments

Add.hack Adds up the two constants 2 and 3 and writes the result in RAM[0]. Recommended

test: ComputerAdd.tst and ComputerAdd.cmp. Alternative test (less thorough but

only requires usage of the built-in RAM16K): ComputerAdd-external.tst

and ComputerAdd-external.cmp.

Program Commen

Max.hack Computes the maximum of RAM[0] and RAM[1] and writes the result in RAM[2].

Recommended test: ComputerMax.tst and ComputerMax.cmp. Alternative test (less

thorough but only requires usage of the built-in RAM16K): ComputerMax-

external.tst and ComputerMax-external.cmp.

Program

Rect.hack Draws a rectangle of width 16 pixels and length RAM[0] at the top left of the screen.

Recommended tests: testComputerRect.tst and ComputerRect.cmp. Alternative test (less thorough but does not require usage of any built-in chips): ComputerRect-

external.tst and ComputerRect-external.cmp.

Before testing your Computer chip on any one of the above programs, read the relevant .tst file and be sure to understand the instructions given to the simulator. The <u>TDL Guide</u> may be a useful reference here.

### Resources

See Chapter 5, the HDL Guide, the TDL Guide, (for reference), and the Hack Chip Set.

The tools that you need for this project are the supplied hardware simulator and the files listed above. If you've downloaded the Nand2Tstris Software Suite, these files are stored in your projects/05 folder.

#### Tips

Complete the computer's construction in the following order:

**Memory:** This chip includes three chip-parts: RAM16K, Screen, and Keyboard. The Screen and the Keyboard are available as built-in chips, and thus there is no need to implement them. Although the RAM16K chip was built in Project 3, we recommend using its built-in version, as it provides a debugging-friendly GUI.

**CPU:** This chip can be constructed according to the proposed CPU implementation given in Figure 5.9 of Chapter 5, using the ALU and register chips built in Projects 2 and 3, respectively. We recommend though using built-in chip-parts instead, in particular ARegister and DRegister. The built-in versions of these two chips have exactly the same interface and functionality as those of the Register chip specified in Chapter 3; however, they feature GUI side-effects that come handy for testing purposes.


In principle, your CPU implementation may include internal chips of your own specification, i.e. chips not mentioned in Figure 5.9 of Chapter 5. However, this is not recommended, and will most likely yield a less efficient CPU design. If you choose to create new chips not mentioned in the book, be sure to document and unit-test them carefully before you plug them into the architecture.

Instruction memory: Use the built-in ROM32K chip.

**Computer:** The top-most Computer chip can be constructed according to the proposed implementation shown in Figure 5.10 of Chapter 5.
 
#### Tools

All the chips mentioned in this project, including the topmost Computer chip, can be implemented and tested using the supplied hardware simulator. Here is a screen shot of testing the Rect.hack program on a Computer chip implementation.



© 2017 Shimon Schocken and Noam Nisan

The Rect program illustrated above draws a rectangle of width 16 pixels and length RAM[0] at the top-left of the screen. Now here is an interesting observation: normally, when you run a program on some computer, and you don't get the desired result, you conclude that the program is buggy. In our case though, the supplied Rect program is bug-free. Thus, if running this program yields unexpected results, it means that the computer platform on which it runs (Computer.hdl and/or some of its lower-level chip parts) is buggy. If that is the case, you have to debug your chips.